

Finite State Machine & Miniwatch Example

Hsi-Pin Ma

<https://eeclass.nthu.edu.tw/course/18498>


Department of Electrical Engineering
National Tsing Hua University

Clocks

- Use signal (100MHz) from crystal (W5)
- Do not use gated clock
 - ex: en & clk (X)
 - For large blocks, use PLL IP
- Various clock frequencies in labs
 - 100-Hz for Debounce circuits
 - 1-Hz for second clock display
 - faster clock for push-button-controlled FSM (~10-Hz) - one pulse generation

“Turn off” a Block

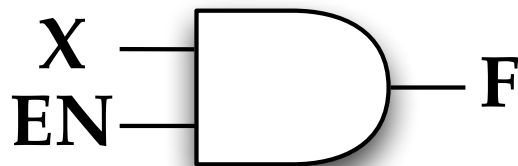
- Enable control (with AND gate) for combinational logics (block input)



$$F = EN \cdot X$$

E	X	F
0	0	0
0	1	0
1	0	0
1	1	1

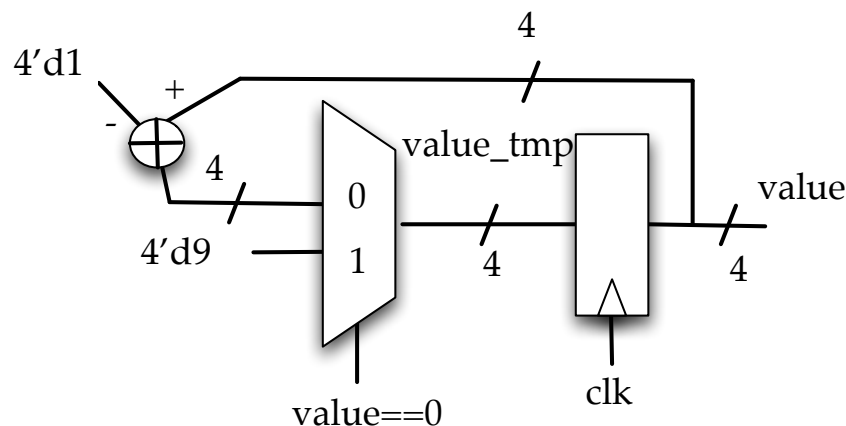- Use MUXs in front of DFFs for unchanged states
 - Clock gating is NOT preferred



Finite State Machine


- Derive the state diagram
- Determine # of DFFs (for N states)
 - Use $\lceil \log_2 N \rceil$ numbers of DFFs for binary-coded state
 - If FSM is Moore model, use DFFs for outputs
 - Write Verilog codes for DFFs
- Use combinational logics for state transitions and output functions (Use *case* statement)

Bad Coding Style:

Inferred Latches in Combinational Logics

- Incomplete case statement
- To avoid
 - Make sure to have *default* case
 - Or always specify the default value in the beginning of the always block

```
always @*  
begin  
  case (alu_control)  
    2'd0: y = x + z;  
    2'd1: y = x - z;  
    2'd2: y = x * z;  
  endcase  
end
```




```
always @*  
begin  
  case (alu_control)  
    2'd0: y = x + z;  
    2'd1: y = x - z;  
    2'd2: y = x * z;  
    default: y = 0;  
  endcase  
end
```

```
always @*  
begin  
  y=0;  
  case (alu_control)  
    2'd0: y = x + z;  
    2'd1: y = x - z;  
    2'd2: y = x * z;  
  endcase  
end
```

Bad Coding Style: Inferred Latches in Combinational Logics
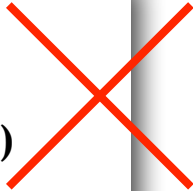
```
always @*  
begin  
    if (alu_control==2'b00)  
        y=x+z;  
    else if (alu_control==2'b01)  
        y=x-z;  
    else if (alu_control==2'b10)  
        y=x*z;  
end
```



```
always @*  
begin  
    y=0;  
    if (alu_control==2'b00)  
        y=x+z;  
    else if (alu_control==2'b01)  
        y=x-z;  
    else if (alu_control==2'b10)  
        y=x*z;  
end
```

```
always @*  
    if (alu_control==2'b00)  
        y=x+z;  
    else if (alu_control==2'b01)  
        y=x-z;  
    else if (alu_control==2'b10)  
        y=x*z;  
    else  
        y=0;
```


Miniwatch Example

Specification

• Function







- Normal function
 - minute-second time display
 - timer supporting up to 59:59
 - alarm for a certain minute
- Tuning function for all normal function
- Using two push buttons for control (one additional reset with DIP switch)

I/O Description

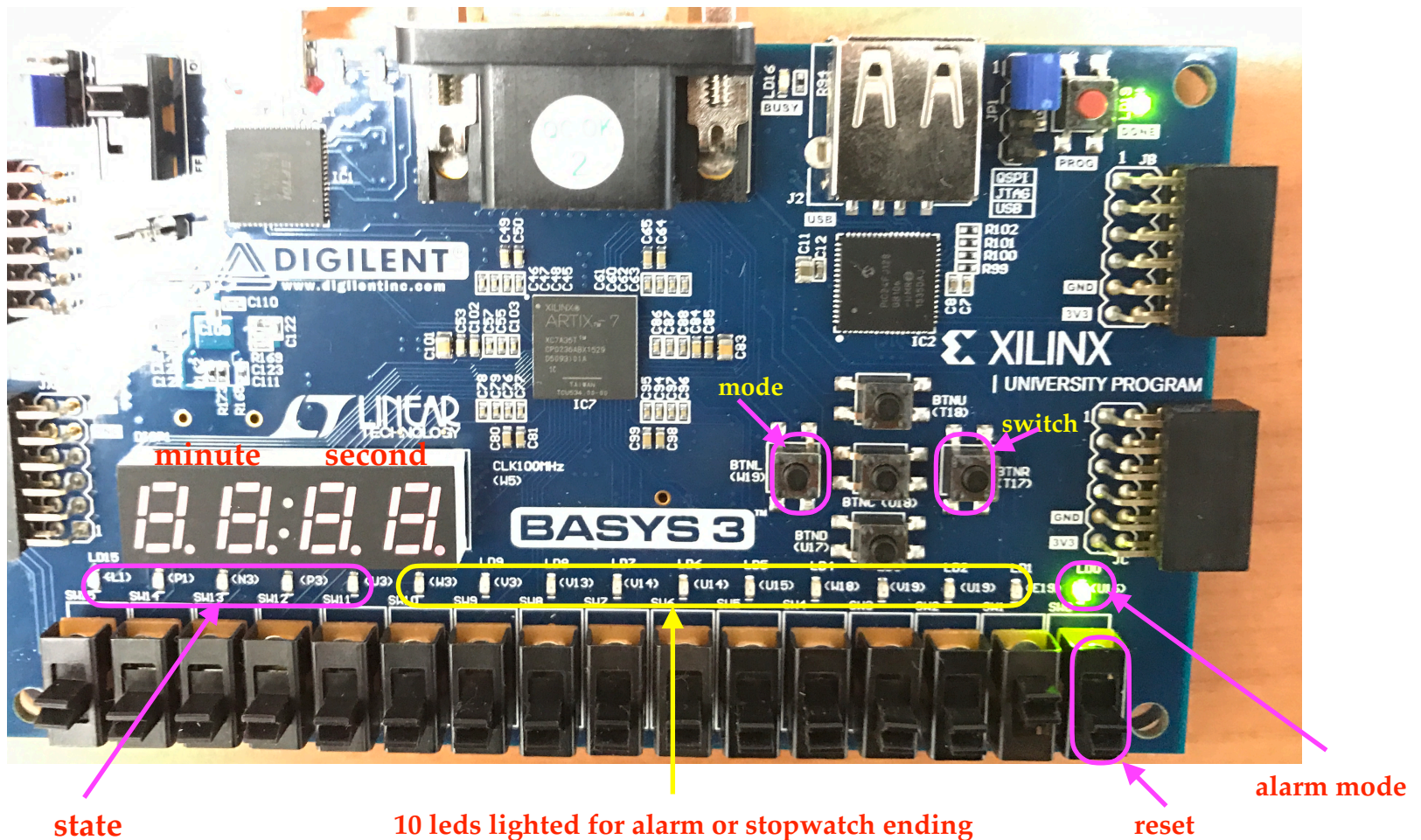

Function Sketch

Control

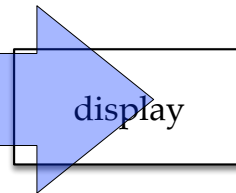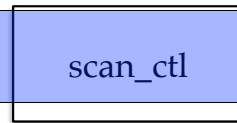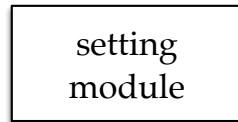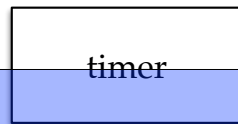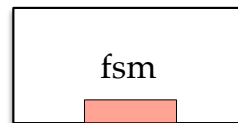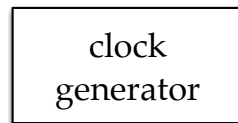


Datapath

Block Diagram




Timedisplay

• Based on counterx

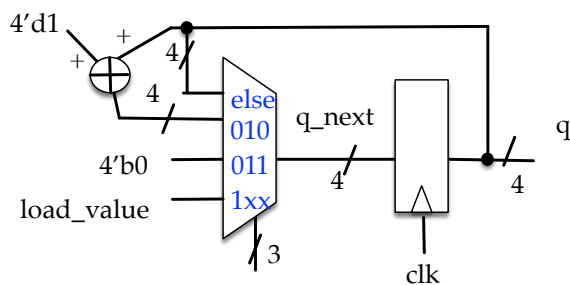

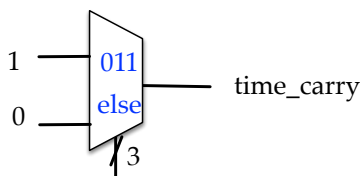{load_value_enable==1, count_enable ==1, q==4'd9}



{load_value_enable==1, count_enable ==1, q==4'd9}


counterx

1'b1
load_value_enable
load_value_sec0
4'd9
clk
rst_n

load_value_sec1
4'd5


load_value_min0
4'd9

load_value_min1
4'd5

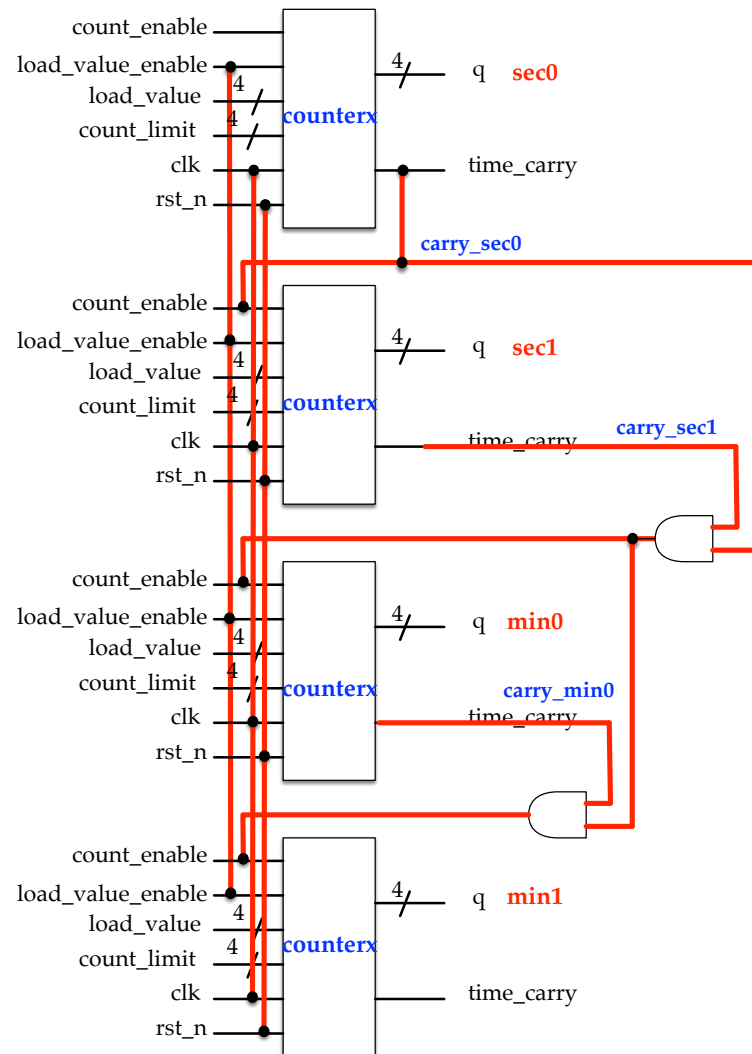


Timer

• Based on downcounter

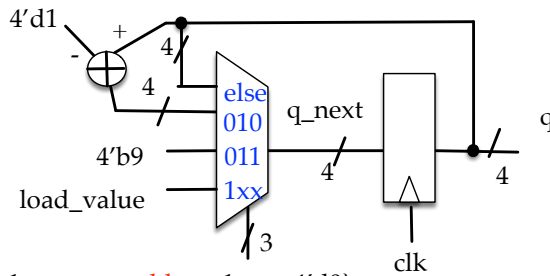

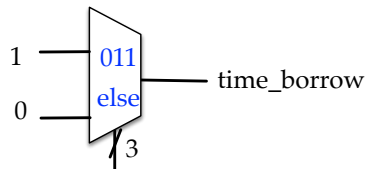{load_value_enable==1, count_enable==1, q==4'd0}



{load_value_enable==1, count_enable==1, q==4'd1}


downcounter

count_enable & (~all_zero)
load_value_enable
load_value_sec0
4'd9
clk
rst_n

load_value_sec1
4'd5


load_value_min0
4'd9

load_value_min1
4'd5

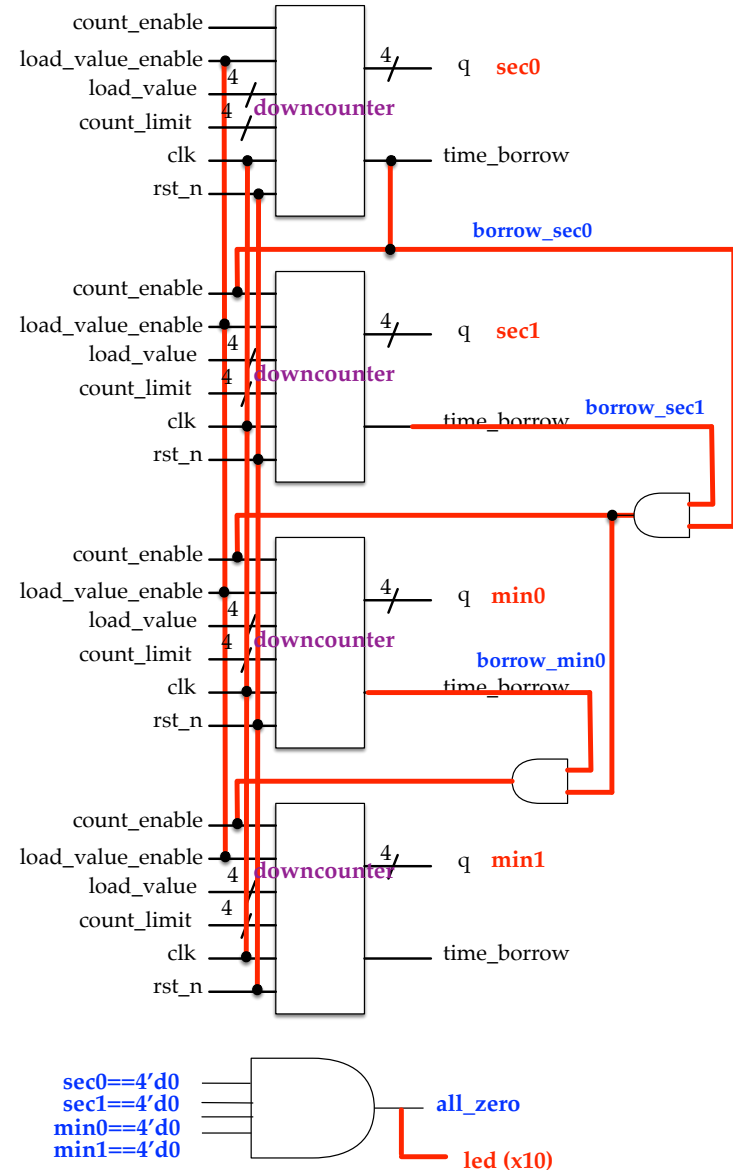


sec0==4'd0
sec1==4'd0
min0==4'd0
min1==4'd0
all_zero
led (x10)


Alarm

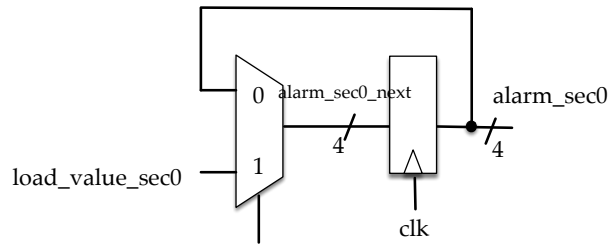


load_value_enable == 1

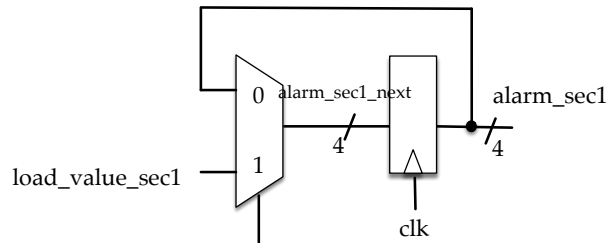


load_value_enable == 1

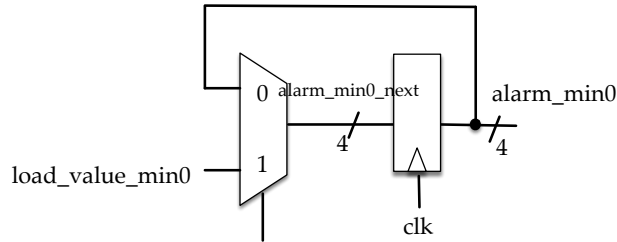

load_value_enable == 1

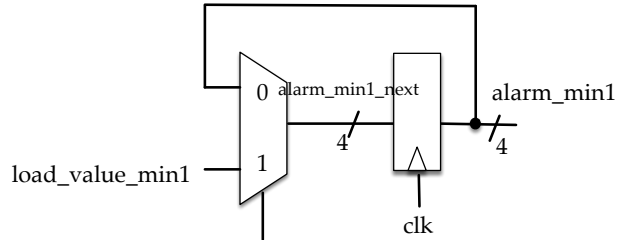


load_value_enable == 1

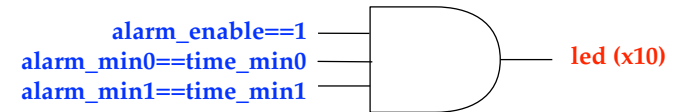


Unitset (Setting Function)

• Based on counterx

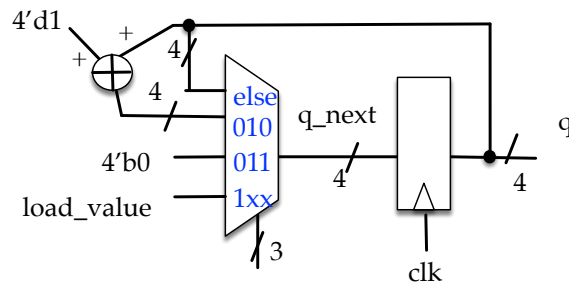


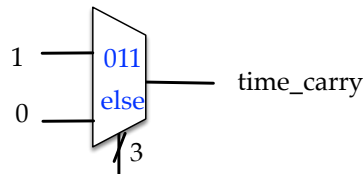{load_value_enable==1, count_enable==1, q==4'd9}



{load_value_enable==1, count_enable==1, q==4'd9}

counterx


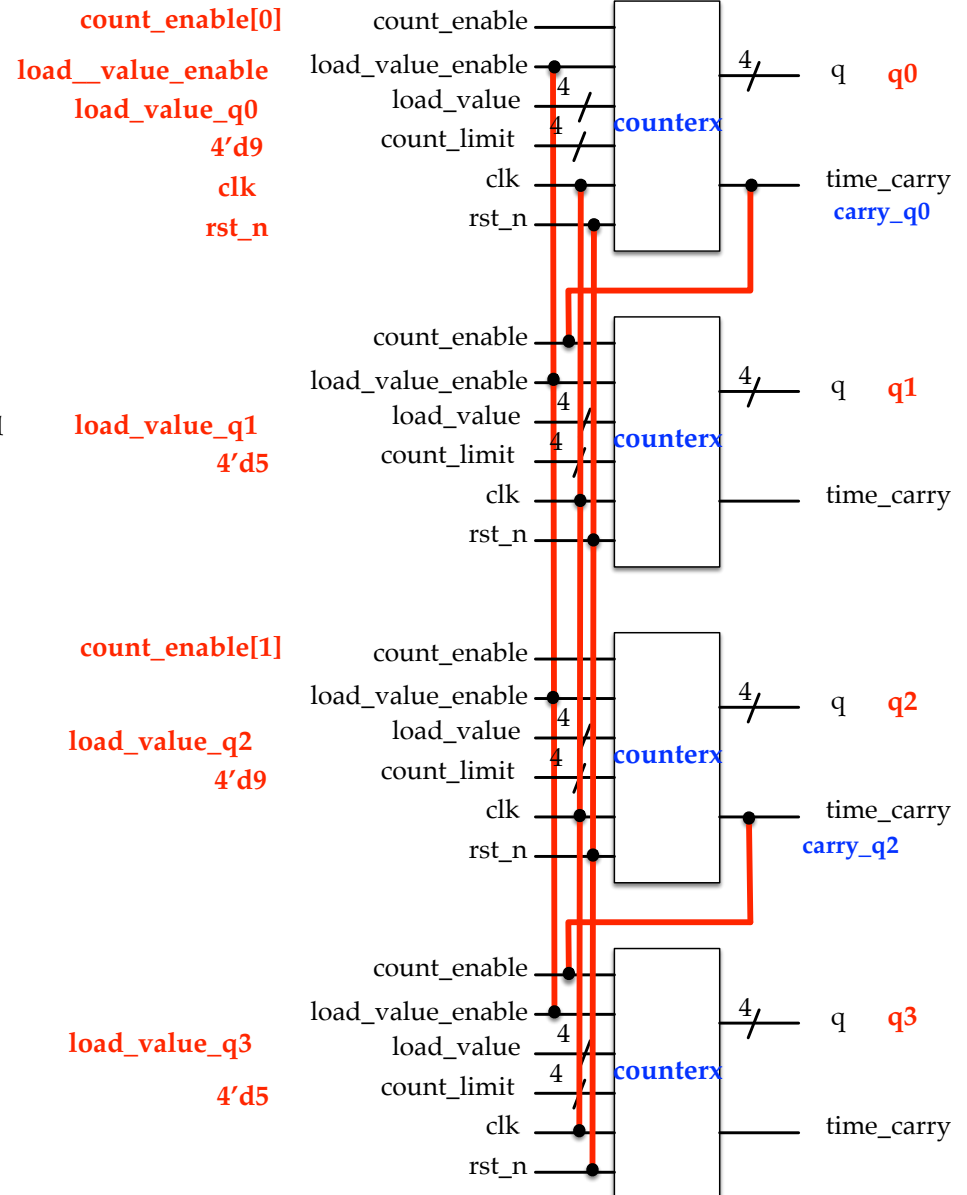


FSM

blue: state

black: input

red: output

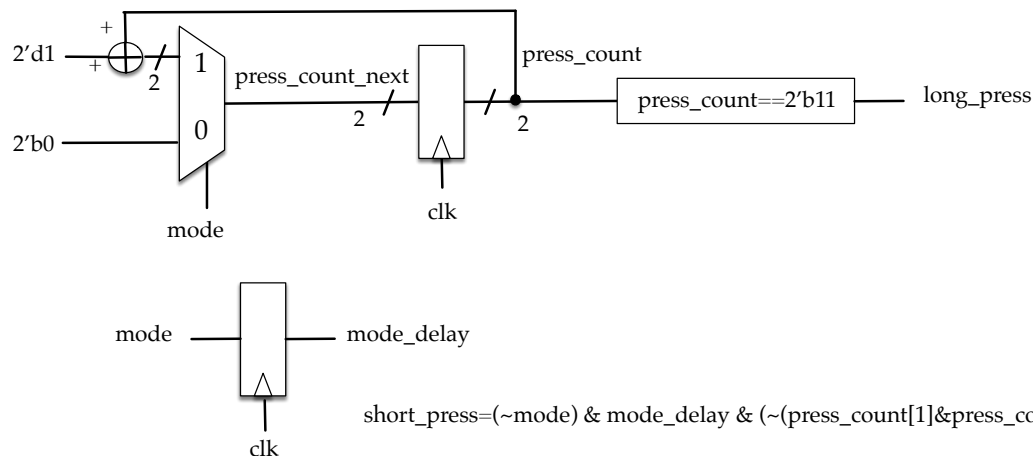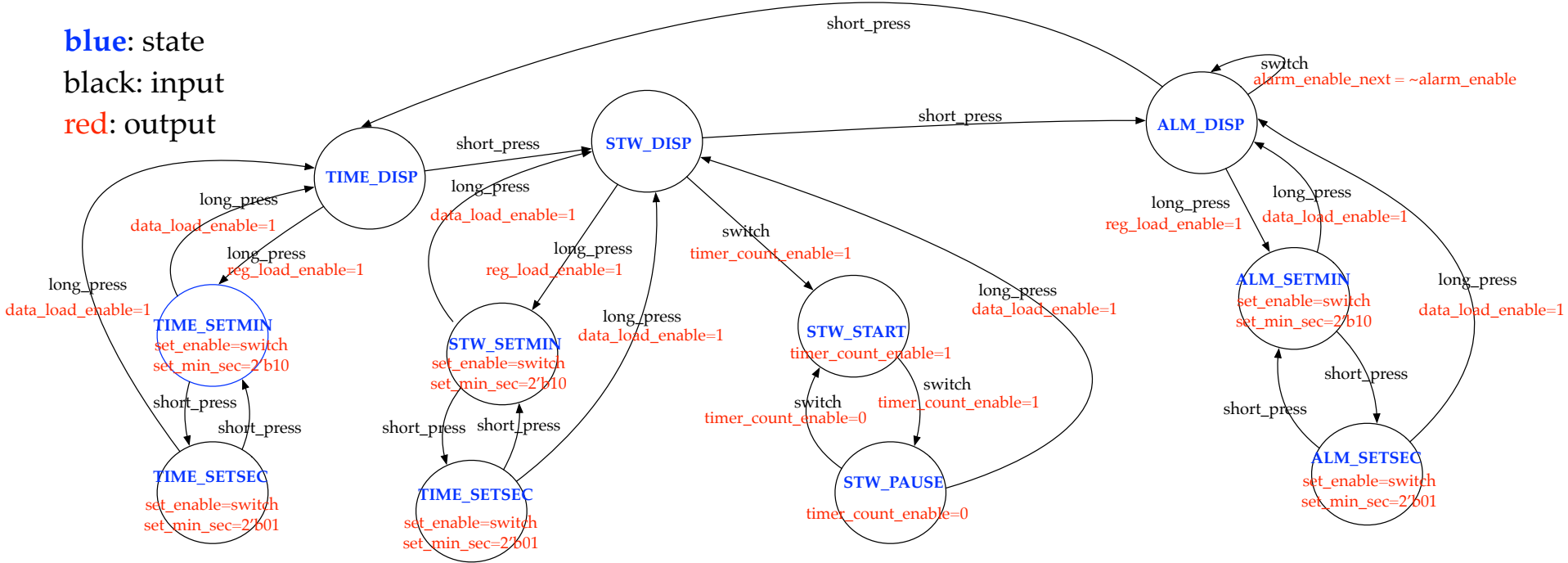

scan_ctl

use 2kHz for scan frequency

